


## Title of the Exercise: Open and Short Circuit Test on Single Phase Transformer

**Date:** 25.10.2020


**Aim:** To perform open and short-circuited test on a two winding Transformer and find out equivalent circuit parameter as well as predetermination of efficiency under various loaded condition.

**Tool used:** MATLAB/Simscape Power System


### Electrical Circuit

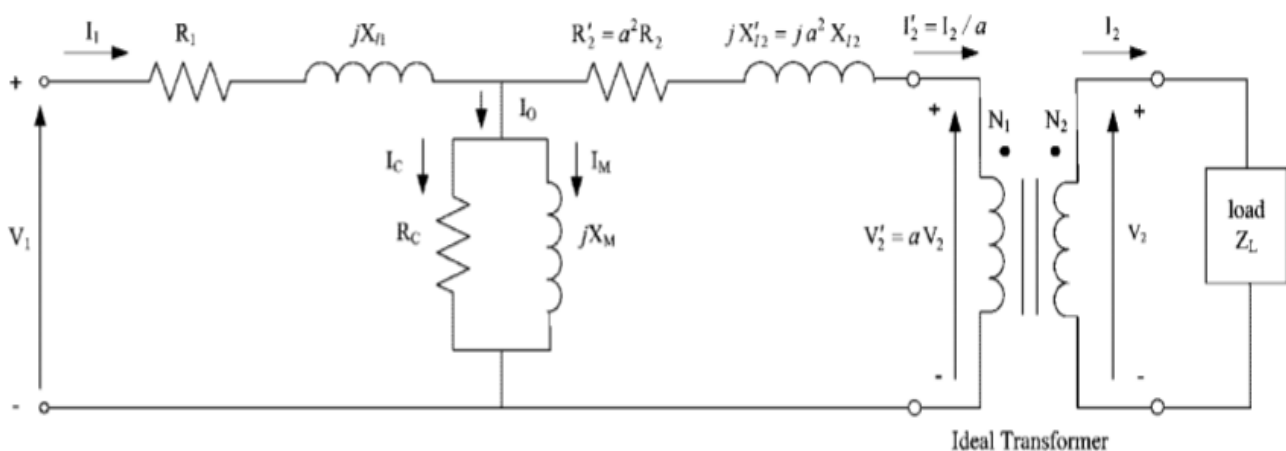

### Open Circuit Test

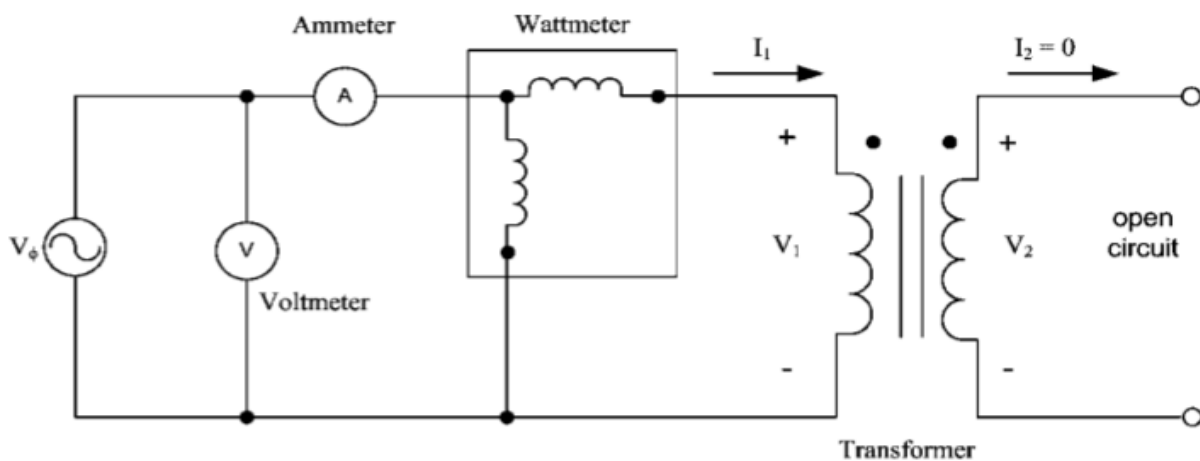

## Short Circuit Test

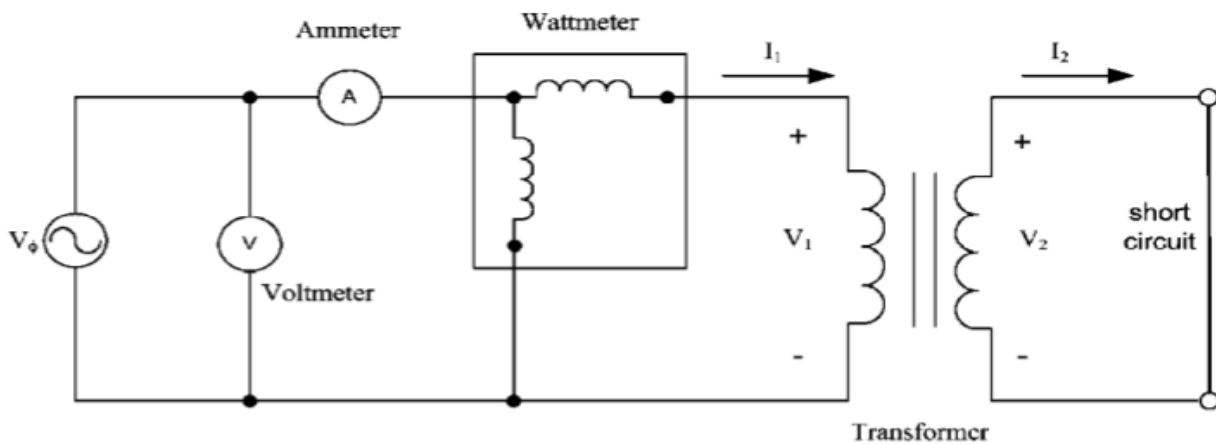

### Parameters used for the study

Transformer rating = 50KVA

$V_1 = 2400$ Volts	Primary Voltage in RMS
$V_2 = 240$ Volts	Secondary Voltage in RMS
$f = 50$ Hz	Frequency
$R_1 = 0.7488$ Ohms	Primary winding resistance
$R_2 = 0.007488$ Ohms	Secondary winding resistance
$X_{11} = 1.00224$ Ohms	Primary winding reactance
$X_{12} = 0.0100224$ Ohms	Secondary winding reactance
$X_M = 5008$ Ohms	Magnetizing reactance
$R_C = 33,391$ Ohms	Resistance for core losses

### Theoretical Analysis:

#### For Open Circuit

$$|Y_E| = G_c - jB_M = \frac{I_{oc}}{V_{oc}}$$

$$PF_{oc} = \cos\theta = \frac{P_{oc}}{V_{oc}I_{oc}}$$

$$G_c = |Y_E|\cos\theta, \quad R_c = \frac{1}{G_c}$$

$$B_M = |Y_E|\sin\theta, \quad X_M = \frac{1}{B_M}$$

### For Short Circuit

$$|Z_{eq}| = |Z_{sc}| = \frac{V_{sc}}{I_{sc}}$$
$$R_{eq} = R_{sc} = \frac{P_{sc}}{I_{sc}^2}$$
$$X_{eq} = X_{sc} = \sqrt{|Z_{eq}|^2 - R_{eq}^2}$$
$$R_{eq} = R_1 + a^2 R_2$$
$$X_{eq} = X_{11} + a^2 X_{12}$$

### For predetermination of efficiency

$P_c = W_{oc} = P_{oc}$  = Iron losses

$P_{sc}$  = full load copper losses

$W_{sc} = \{ (I_L / I_f)^2 \} * P_{sc} = P_{cu}$

$W_{sc}$  = copper losses at different loaded conditions

$W_T = P_c + P_{cu}$  – Total power losses

$I_L$  = Load current

$I_F$  = Full load current

$\cos \Phi$  = Power factor

Efficiency =  $(P_o / P_i) * 100$

### **Calculations (Predetermination)**

$I_f = 207.4$  A (From short circuit test) (Current at full load)

$W_{oc} = 174.3$  W (From open circuit test) (Iron losses)

We calculate efficiency of transformer at different load current as 1, 2, ..... 10 and power factor as 1

At  $I_L = 1$  A

$W_{sc} = P_{cu} = \{ (1 / 207.4)^2 \} * 644.2 = 0.0149$  Watts

Power output =  $I_L * 240 = 1 * 240 = 240$  Watts

Total Power Loss =  $174.3 + 0.0149 = 174.3149$  Watts

Power Input = Power output + Total power loss

$$= 240 + 174.3149 = 414.3149$$

$$\text{Efficiency} = (240/414.3149) \times 100 \% = 57.9269\%$$

Therefore, efficiency of transformer at load current 1 is 57.92%

At  $I_L = 2A$

$$W_{sc} = P_{cu} = \{(2/207.4)^2\} \times 644.2 = 0.0599 \text{ Watts}$$

$$\text{Power output} = I_L \times 240 = 2 \times 240 = 480 \text{ Watts}$$

$$\text{Total Power Loss} = 174.3 + 0.0599 = 174.3599 \text{ Watts}$$

Power Input = Power output + Total power loss

$$= 480 + 174.3599 = 654.3599$$

$$\text{Efficiency} = (480/654.3599) \times 100 \% = 73.33541\%$$

Therefore, efficiency of transformer at load current 1 is 73.35%


Now, similarly we can find efficiency for load current 3,4...10.

### **Procedure for simulation study**


- Initialize the input parameters and write coding as per the requirement of plots in m file and save it.
- Open new Simulink and make mathematical modelling as per circuit diagram and save it.
- Run Simulink file and then run m file.
- Calculate the equivalent parameters and plot the necessary graphs.

### **Simulation Diagram and m. file coding**

For Open Circuit

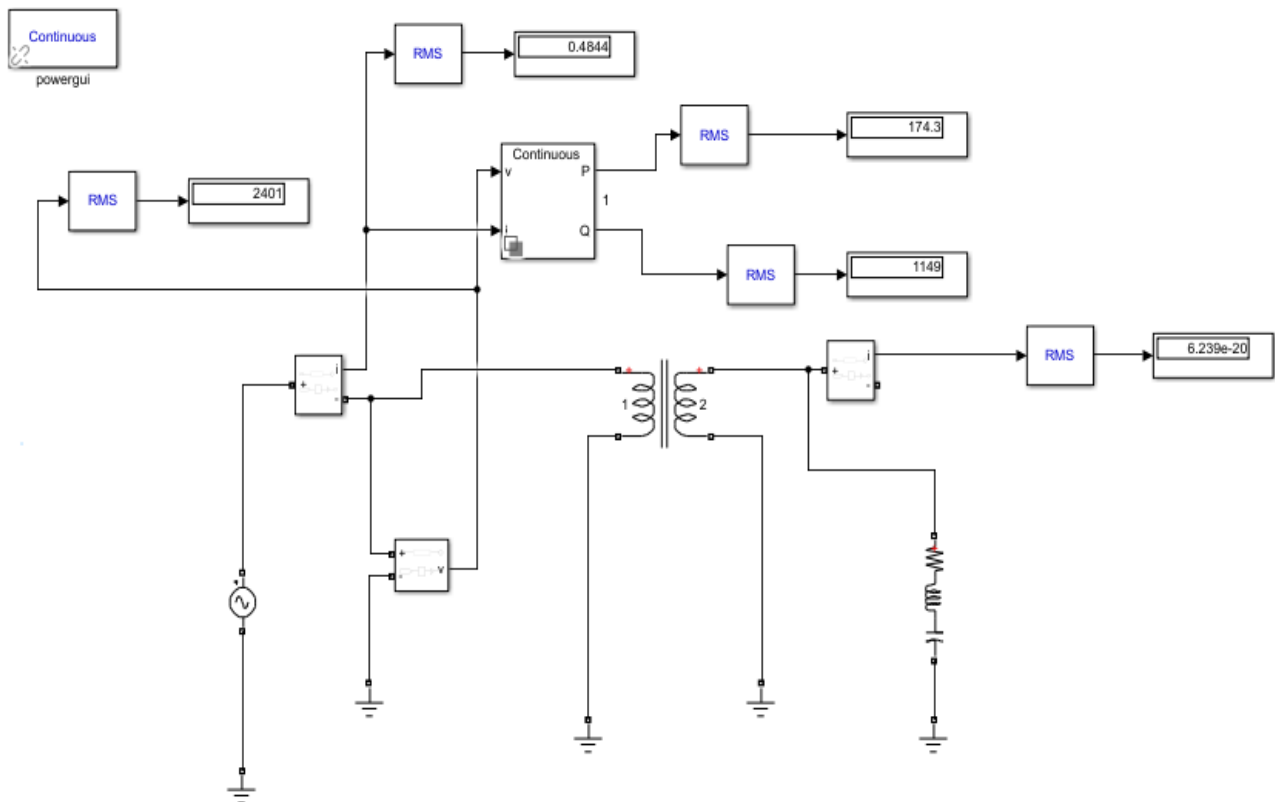

For Short Circuit

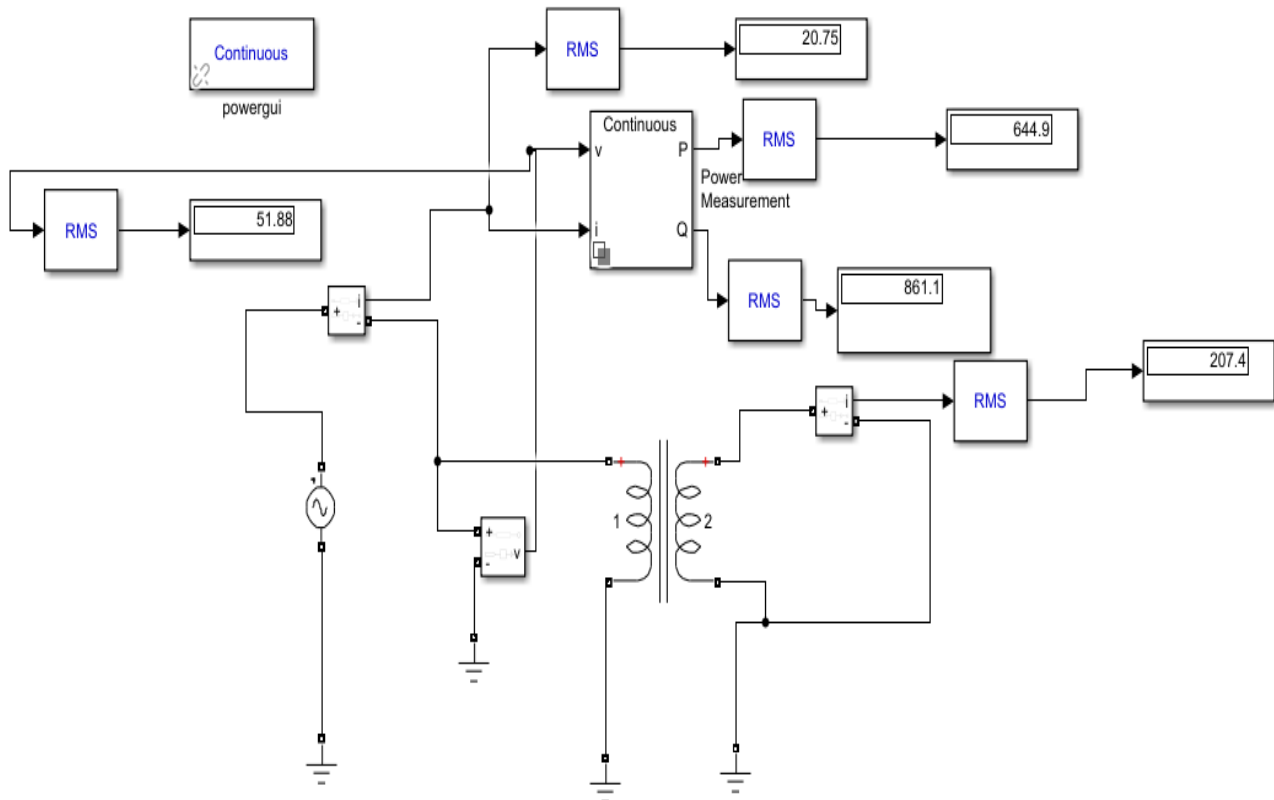

## M file coding –


```
%Open Circuit
Poc = 174.3;
Voc = 2400;
Ioc = 0.4844;
PFoc=Poc/(Voc*Ioc);

%Short Circuit
Isc = 207.4;
Vsc = 51.9;
Psc = 644.2;
iL = (0:1:10);

pfi = (0.1:0.1:1);
for i = 1:10
    pf = pfi(i);
    Po = (240*iL)*pf;
    Wsc = ((iL/Isc).^2)*Psc;
    Wt = Wsc + Poc;
    Pi = Po + Wt;
    Eff = 100*(Po./Pi);
    plot(iL, eff);
    hold on
end
hold off
xlim([-1 101])
legend("pf is "+string((0.1:0.1:1)))
xlabel('iL');
ylabel('Efficiency');
```
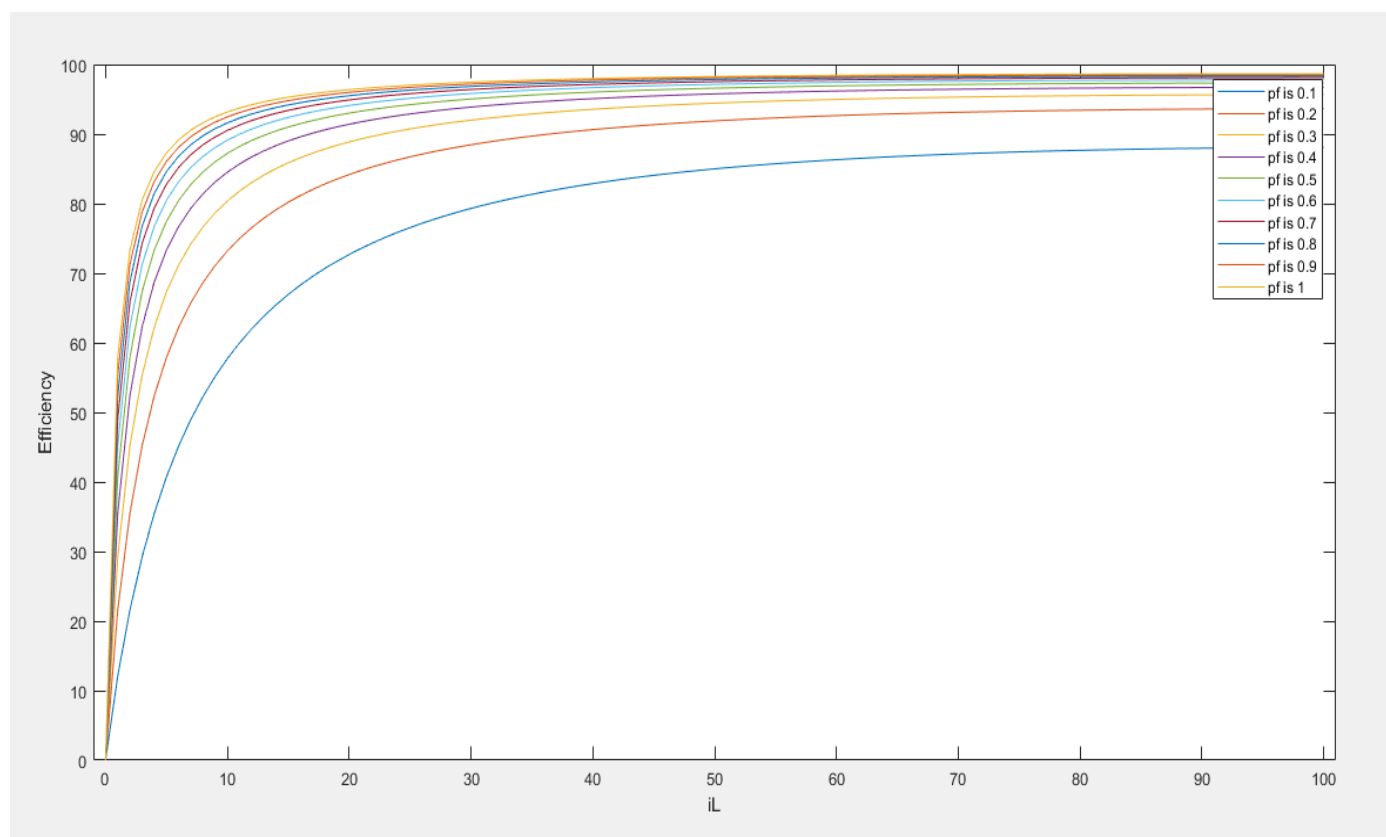
## Results and Discussions-

This section contains waveforms of different speed control characteristics.



## Comparison (Observations)

S.No	Load Current( $I_L$ )	Constant Losses( $W_{oc}$ )	Copper Losses( $W_{sc}$ )	Total Losses( $W_T$ )	O/P Power(w)	I/P Power(w)	% $\eta$
1	1	174.3	0.0150	174.3150	240	414.3	57.9269
2	2	174.3	0.0599	174.3599	480	654.4	73.3541
3	3	174.3	0.1348	174.4348	720	894.4	80.4978
4	4	174.3	0.2396	174.5396	960	1134.5	84.6158
5	5	174.3	0.3744	174.6744	1200	1374.7	87.2934
6	6	174.3	0.5391	174.8391	1440	1614.8	89.1730
7	7	174.3	0.7338	175.0388	1680	1855.0	90.5644
8	8	174.3	0.9585	175.2585	1920	2095.3	91.6355
9	9	174.3	1.2131	175.5131	2160	2335.5	92.4850
10	10	174.3	1.4976	175.7976	2400	2575.8	93.1750

**Conclusion:**

Open circuit and short circuit test have been done and equivalent circuit parameter as well as predetermination of efficiency under various loaded condition has also been obtained.

**Inference:**

Our predetermined values match with the simulation value which are tabulated in above table.

**References:**

- <https://in.mathworks.com/>